
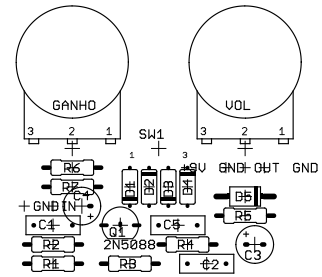
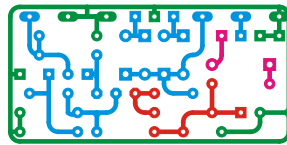


Lovepedal EnglishMan

Esquema: Lovepedal
Layout: André Freitas

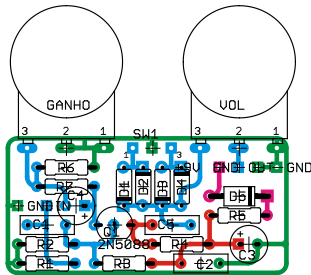

Lista:

Resistores	Capacitores	Transistor	Outros	Diodos
R1-2M2	C1-470nF	2N5088	Sw1-On-Off-On	D1/D2-1N4148
R2-470K	C2-100nF		Ganho-1kB	D3/D4-BAT46
R3-2M2	C3-47uF		100k-B	D5-Schotty (eu usei 1N4007 e funcionou bem)
R4-3K3	C4-47uF			
R5-100R	C5-220nF			
R6-330R				
R7-330R				

